


Synchronous detection

Laurea Specialistica in Fisica
A.A. 2007/08

Dr. Francesco Quochi

Detection of an AC signal

- rectifier + low-pass (e.g., RC) filter

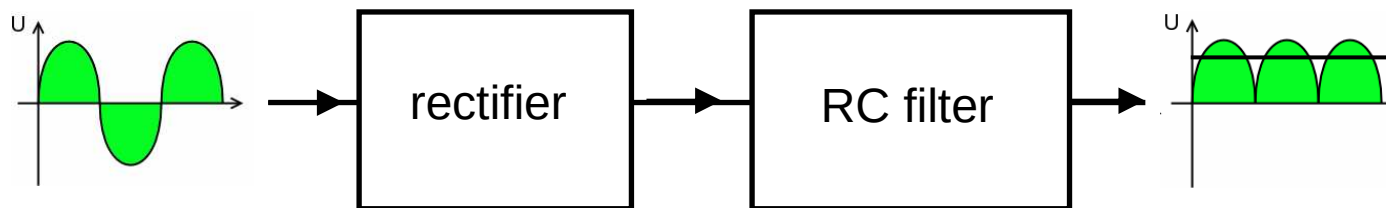

Filtered noise: $\sigma_{\text{noise}}^2 = \int_0^B S(f') df'$

$$B = 1 / 2\pi RC$$

- band-pass filter



Filtered noise:

$$\sigma_{\text{noise}}^2 = \int_{f-B/2}^{f+B/2} S(f') df'$$

$$B = f / Q \gg 1 / 2\pi RC$$

Phase-sensitive detection PSD

PSD to single out the signal at given frequency

Advantages:

- ✓ inherently AC measurement (no rectification)
- ✓ time integration with small bandwidth

signal

$$V_S \sin(2\pi ft + \varphi_S)$$

$$V_R \sin(2\pi ft + \varphi_R)$$

mixer



$$V_{\text{PSD}} = V_S V_R \sin(2\pi ft + \varphi_S) \sin(2\pi ft + \varphi_D) =$$

$$\frac{1}{2} V_S V_R \cos(\varphi_S - \varphi_D) - \frac{1}{2} V_S V_R \cos[2\pi(2f) + \varphi_S + \varphi_D]$$


$$\propto V_S \cos(\Delta\varphi) + \text{sum-frequency term}$$

reference


at same frequency

PSD with low-pass filter

1) $f_S = f_R = f$

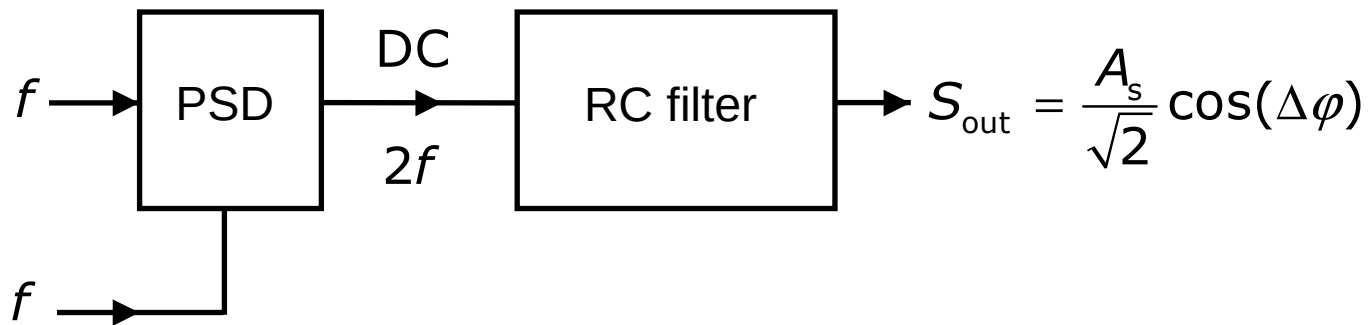


2) $f_S \neq f_R$

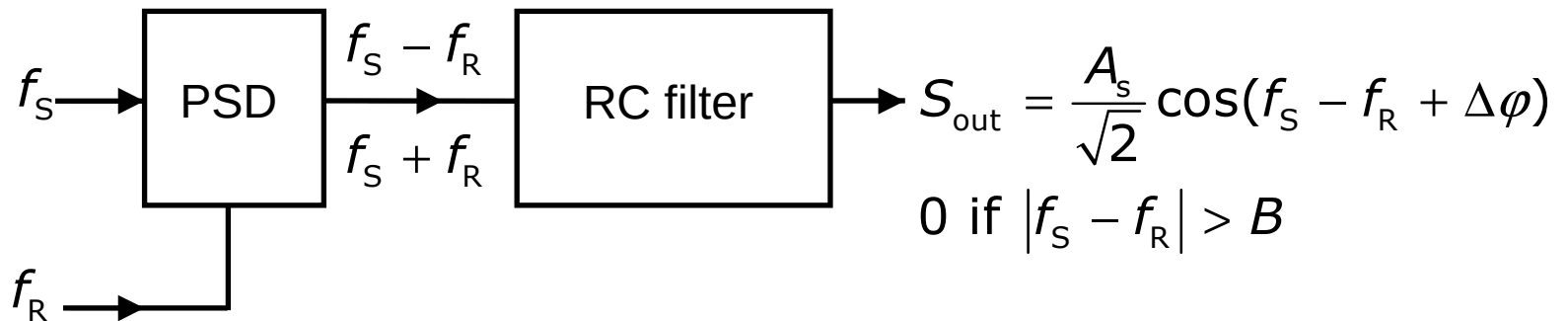

Lock-in amplifier

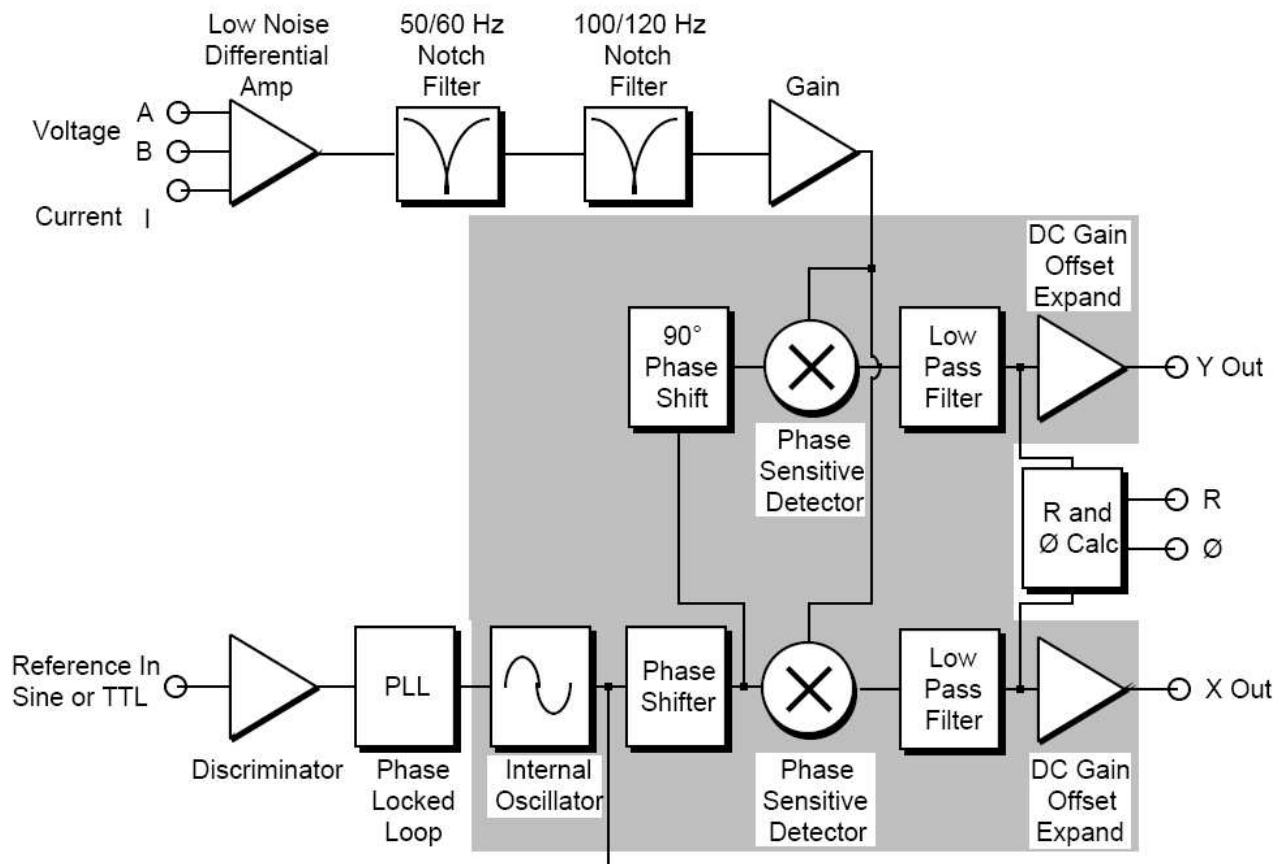- AC amplification
- dual phase detection + integration → amplitude and phase retrieval
- DC amplification



$$X = \frac{V_s}{\sqrt{2}} \cos(\Delta\phi)$$


$$Y = \frac{V_s}{\sqrt{2}} \sin(\Delta\phi)$$

$$R = \sqrt{X^2 + Y^2} = \frac{V_s}{\sqrt{2}}$$

$$\Delta\phi = \tan^{-1} \left(\frac{Y}{X} \right)$$

Lock-in detection

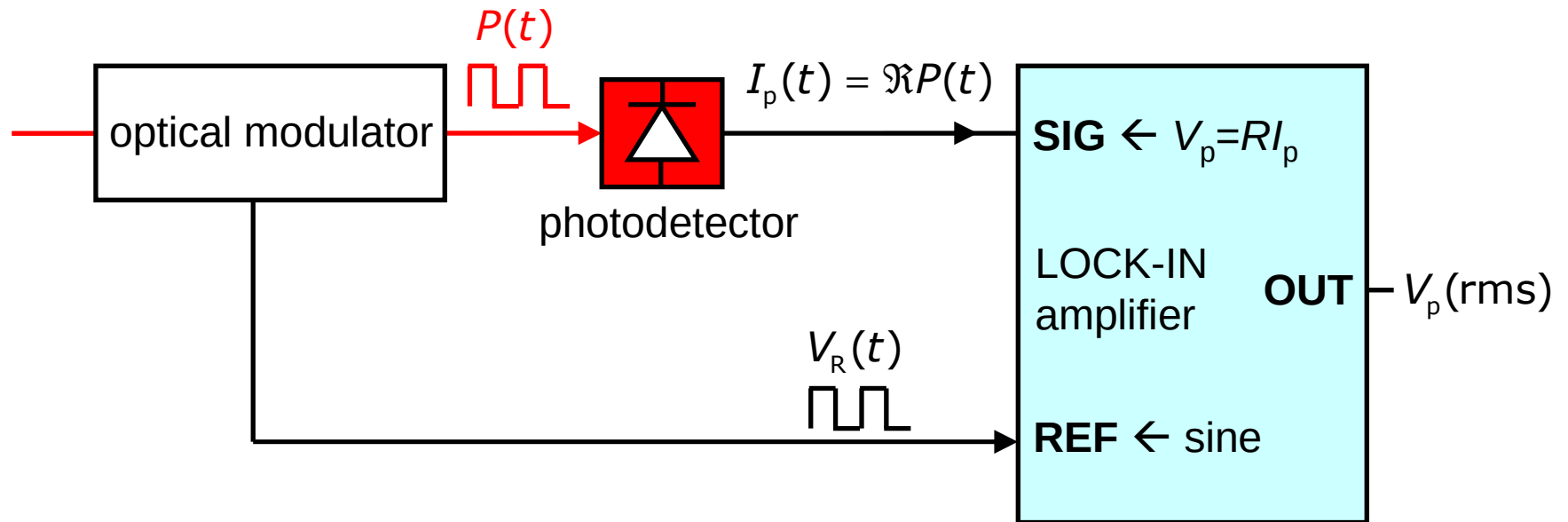- amplitude modulation of the optical signal
- generation of a reference signal at same frequency
- measurement with lock-in amplifier



Noise measurement using lock-in detection

- generation of a reference signal at noise frequency
- measurement of device (photodetector) noise with lock-in amplifier

